


Coordination - Level up! ⁷

Level 0: Basic combos


For the circuit(s) below, say that $V_{bat} = 5V$, $R_1 = 2\Omega$, $R_2 = 3\Omega$, $R_3 = 4\Omega$, $C_1 = 6mF$, $C_2 = 7mF$, and $C_3 = 8mF$. For your given circuit:

- What is the equivalent capacitance or resistance of the circuit?
- Which circuit element would have the largest voltage drop?
- Which circuit element would have the smallest charge or smallest current?


Circuit A:

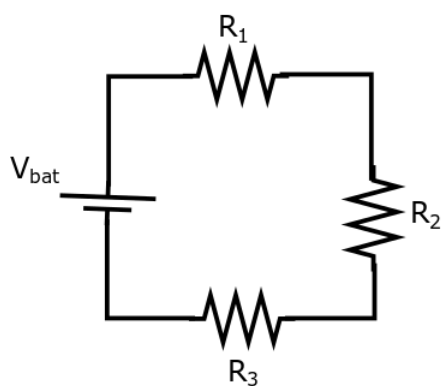


Circuit B:

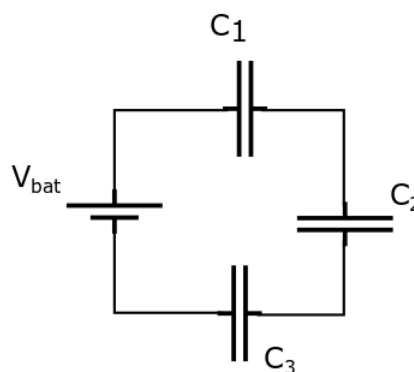

Circuit C:

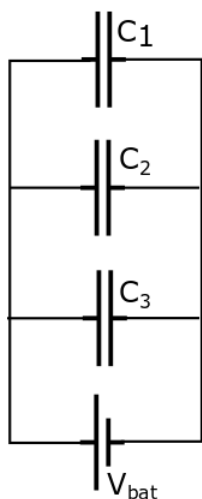

Circuit D:

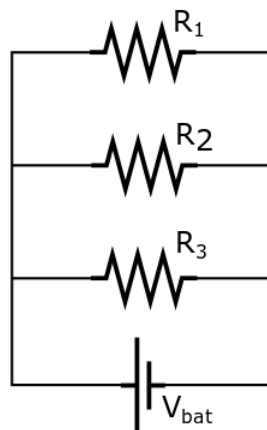


⁷Levels 0 - 2: Modified by Daryl McPadden for Fab Physics from University Modeling Instruction
Levels 3 - Bonus: Written by Daryl McPadden for Fab Physics

Level 1: Equal circuit elements


For the circuit(s) below, say that $V_{bat} = 16V$, all resistors are $R = 150\Omega$ and all capacitors are $C = 470\mu F$. For your given circuit:

- (a) What is the equivalent capacitance or resistance of the circuit?
- (b) Which elements are in series? Which are in parallel? How do you know?


Circuit A:

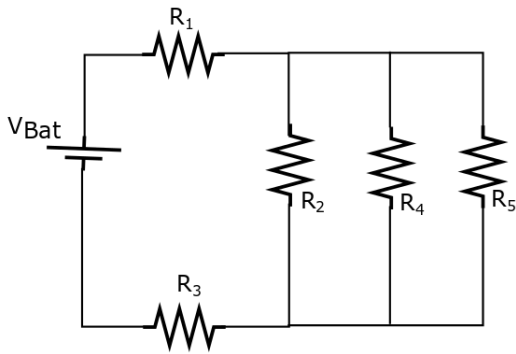


Circuit B:

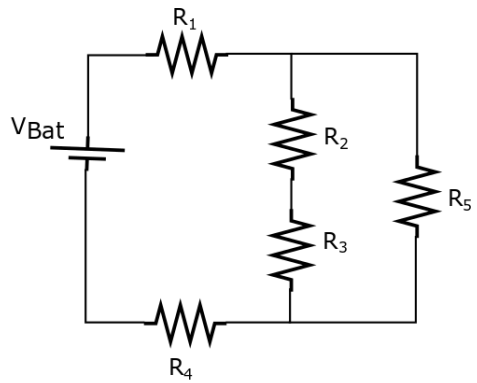

Circuit C:

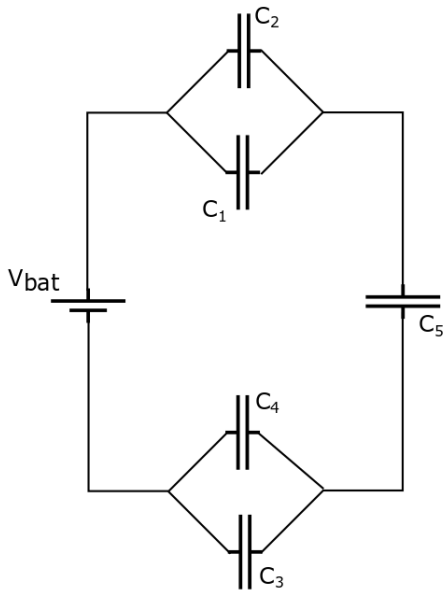

Circuit D:

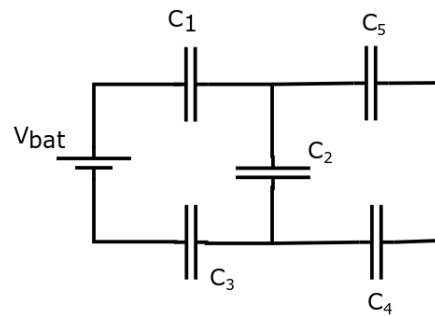


Level 2: Resistor Circuits


For the circuit(s) below, you have been given some of the quantities for various elements around the circuit. For example, V_1 would correspond to the voltage across Resistor 1. For your given circuit,

- (a) Which resistors are in series and which resistors are in parallel? How do you know?
- (b) Find all the missing quantities for each resistor (R , V , I , and P).
- (c) What is the voltage, current, and power provided by the battery in your circuit?
- (d) If the resistors in the circuit were lightbulbs, which would be the brightest?


Circuit A:

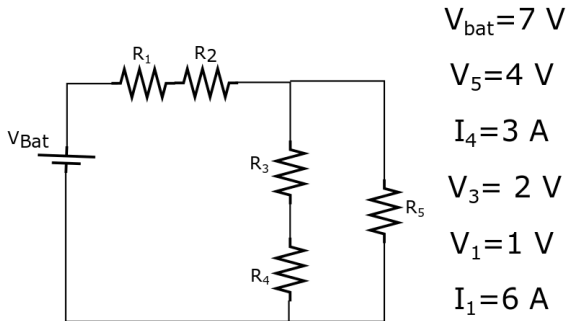


Circuit B:

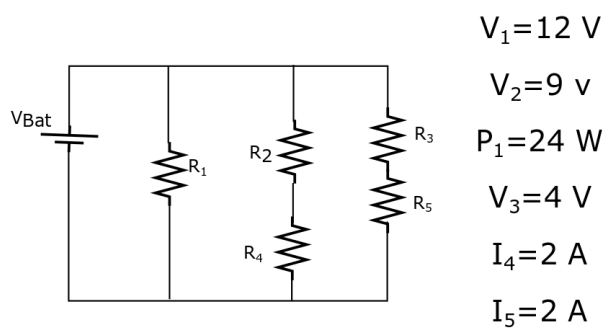

Circuit C:

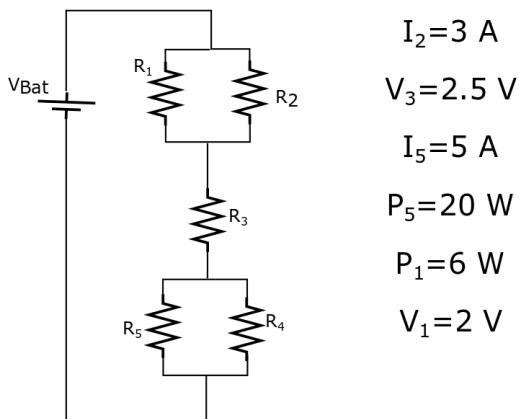

Circuit D:

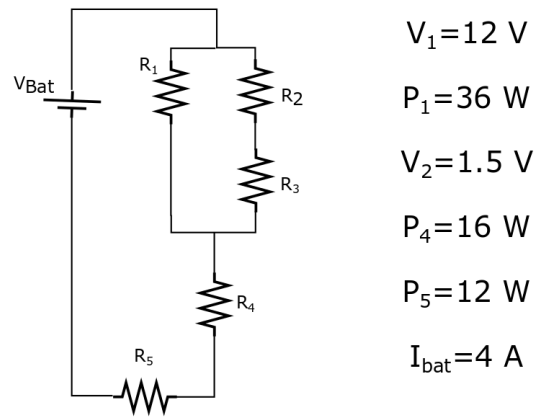


Level 3: Capacitor Circuits


For the circuit(s) below, you have been given some of the quantities for various elements around the circuit. For example, V_1 would correspond to the voltage across Capacitor 1. For your given circuit,

- (a) Which capacitors are in series and which capacitors are in parallel? How do you know?
- (b) Find all the missing quantities for each capacitor (C , V , Q , and U).
- (c) What is the voltage provided by the battery in your circuit?
- (d) What is the total charge stored by the circuit? What is the total energy?


Circuit A:

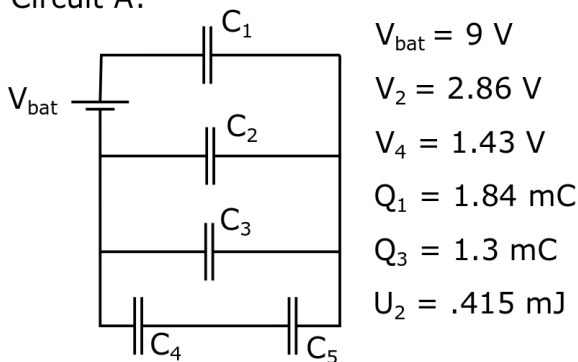

Circuit B:

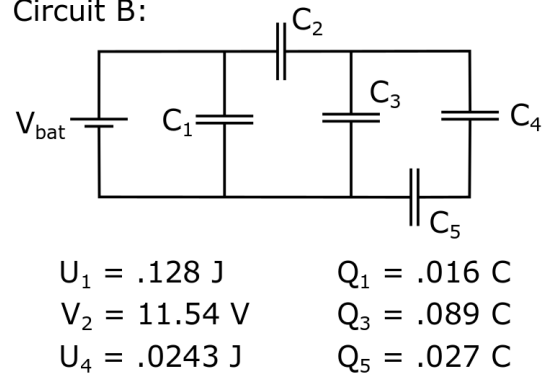


Circuit C:

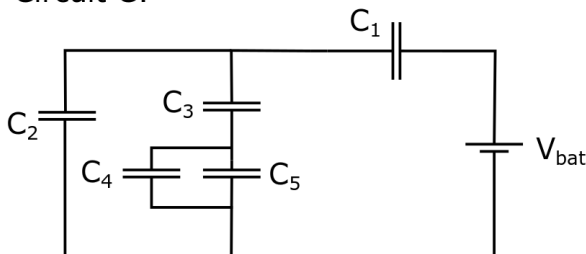

$V_{\text{bat}} = 3 \text{ V}$ $V_3 = .25 \text{ V}$
 $Q_1 = 178 \text{ nC}$ $U_4 = 4.7 \text{ nJ}$
 $U_2 = 74.4 \text{ nJ}$ $V_5 = .97 \text{ V}$

Circuit D:

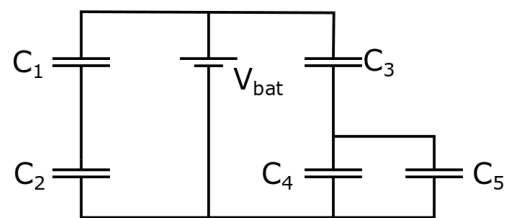


$Q_1 = .034 \text{ C}$ $U_3 = .096 \text{ J}$
 $U_1 = .058 \text{ J}$ $V_4 = 2.97 \text{ V}$
 $V_2 = 1.6 \text{ V}$ $U_5 = .097 \text{ J}$

Level 4: But why do you need multiple batteries?!


For the circuit(s) below, say that $V_{bat1} = 9V$, $V_{bat2} = 6V$, and all resistors are $R = 100\Omega$. For your given circuit:

- Are there places in your circuit that can simplify? (AKA resistors in series or in parallel?)
- Redraw the circuit after making the simplifications that you can.
- How many different currents do you have in your circuit? Draw and label this on your picture. What node rule equations can you make?
- How many different loops do you have in your circuit? What loop rule equations can you make?
- Solve for your unknown currents. Note: you can use Wolfram Alpha or other resources online to solve the system of equations.


Circuit A:

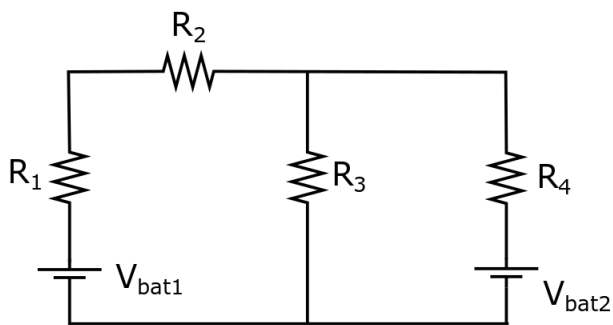


Circuit B:

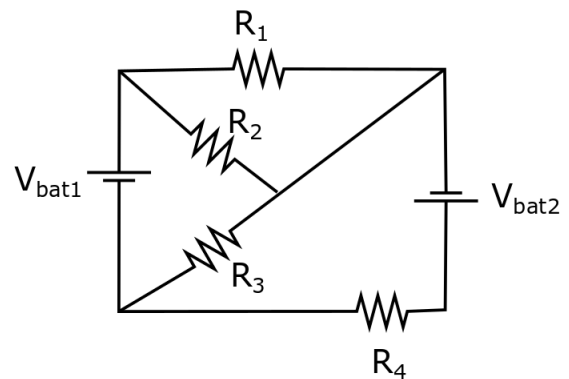

Circuit C:

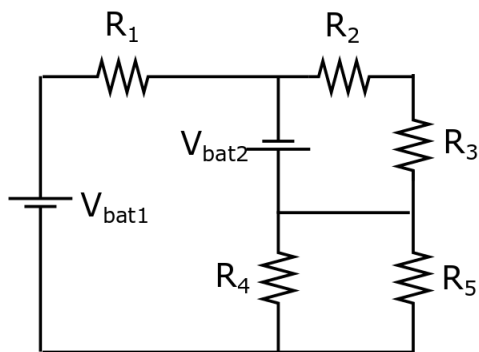

Circuit D:

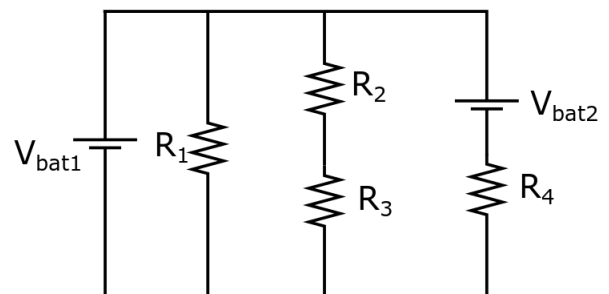

Bonus: Combine all of the things!

Consider the circuit below where initially the capacitors are all uncharged.

- Initially, where is there current in the circuit?
- What is the initial current provided by the battery if $V_{bat} = 6V$, all resistors are $R = 1000\Omega$, and all capacitors are $C = 2200mF$? (At the moment the switch is closed.)
- What would the V vs t , Q vs t , and I vs t graphs look like for each of the capacitors?
- After the switch has been closed for a long time, where is there current in the circuit?
- What is the final current provided by the battery? (After the switch has been closed for a long time.)
- If the switch is then opened again, what would you expect to happen? Explain in words.

